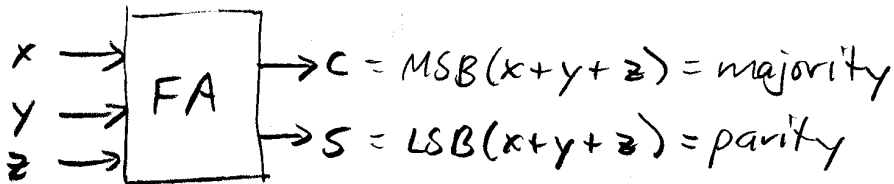


« Sort with $\Theta(\lg N)$ procs in linear array »
 « Firing squad - $\Theta(1)$ -size state »

6.896
 2/9/04
 L2.1

Addition


Basic component: Full adder - combinational



Problem:


Add $\geq N$ -bit numbers

Ripple-carry adder

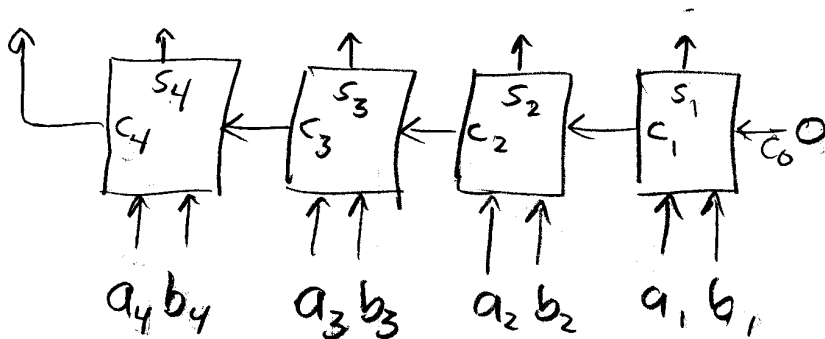

N -bit #'s $\Rightarrow \Theta(N)$ time, $\Theta(N)$ HW, combinational

Serial adder

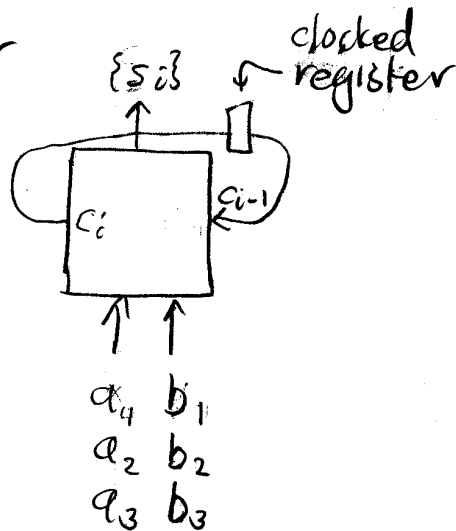

$\Theta(N)$ time, $\Theta(1)$ hardware, sequential (clocked)

6,896
2/9/04
L2,2

Fast addition

Idea: carries are the hard part.

Know carries \Rightarrow compute sum in $\Theta(i)$ time

How? Array of full adders. «Show on ripple-carry adder»

1 0 1 0 1 0 1
1 1 1 0 0 1 1

1 1 0 0 1 0 0 0
g p g k p p g (k)

Classify stages:


kill: 0 \Rightarrow carry-out = 0

propagate: 1 or 0 \Rightarrow carry-out = carry-in

generate: 1 \Rightarrow carry-out = 1


Carry into stage = $\begin{cases} 1 & \text{if most recent non-p is k} \\ 0 & \text{otherwise} \end{cases}$

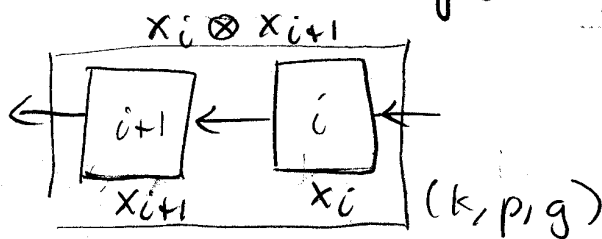When do 2 consecutive stages kill, prop, gen?



\otimes	k	p	g
k	k	k	g
p	k	p	g
g	k	g	g

Associative!

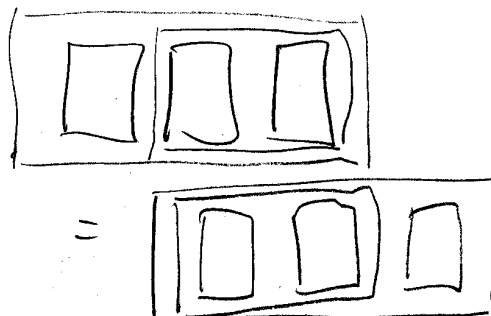

6.896
2/9/04
L2.3

Theorem. Let $x_i =$ carry status of stage i , where $x_0 = k$. Define $y_i = x_0 \otimes x_1 \otimes \dots \otimes x_i$.

Then $y_i = k \Rightarrow c_i = 0$
 $y_i = g \Rightarrow c_i = 1$
 $y_i = p$ does not occur.

Proof. Induction on i . \square

Log-time circuit:


$$y_0 = x_0$$

$$y_1 = x_0 \otimes x_1$$


$$y_2 = x_0 \otimes x_1 \otimes x_2$$

$$y_N = x_0 \otimes x_1 \otimes \dots \otimes x_N$$

Use tree for each calculation:

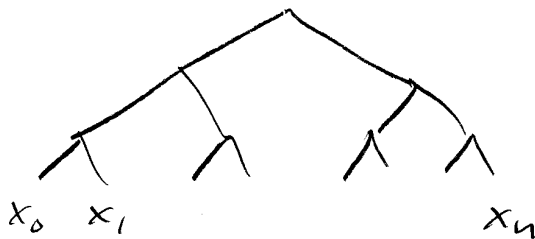

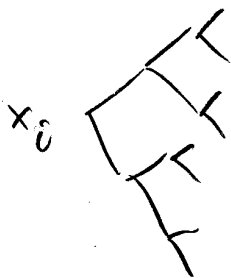Use tree to broadcast inputs (bounded-degree network):



Time = $\Theta(\lg N)$, HW = $\Theta(N^2)$.

Carry-lookahead addition

G.896
2/9/04
L2.4

$\Theta(\lg N)$ time, $\Theta(N)$ HW.

"Parallel prefix"


Let $[i, j]$ denote $x_i \otimes x_{i+1} \otimes \dots \otimes x_j$

Lemma. $[i, j] \otimes [j+1, k] = [i, k] \boxtimes$


$$x_i = [0, i]$$

$$y_i = [0, i]$$

Build tree:

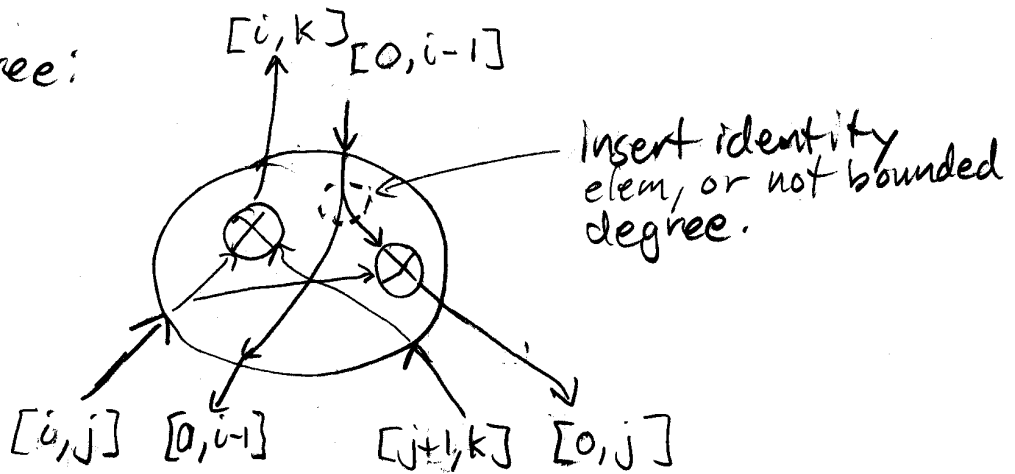


Globally:

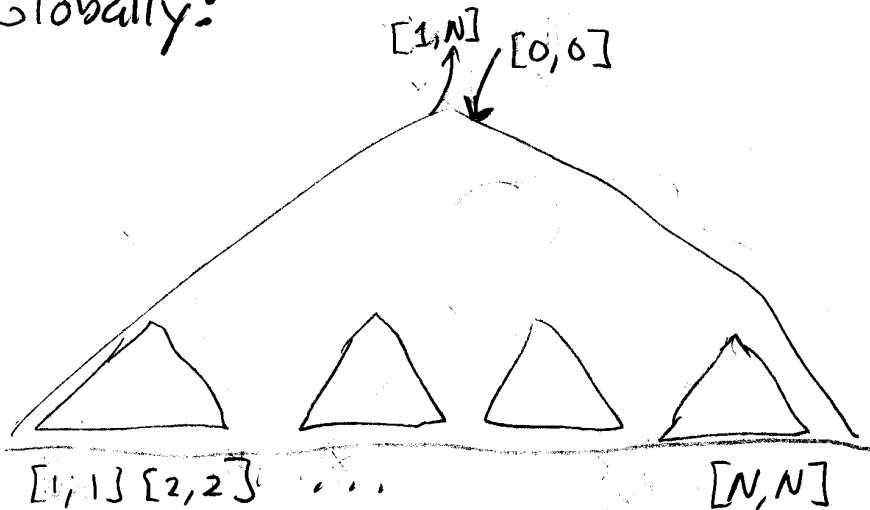


Left child values are passed up.

6.896
2/9/04
L2.5

Similar method:

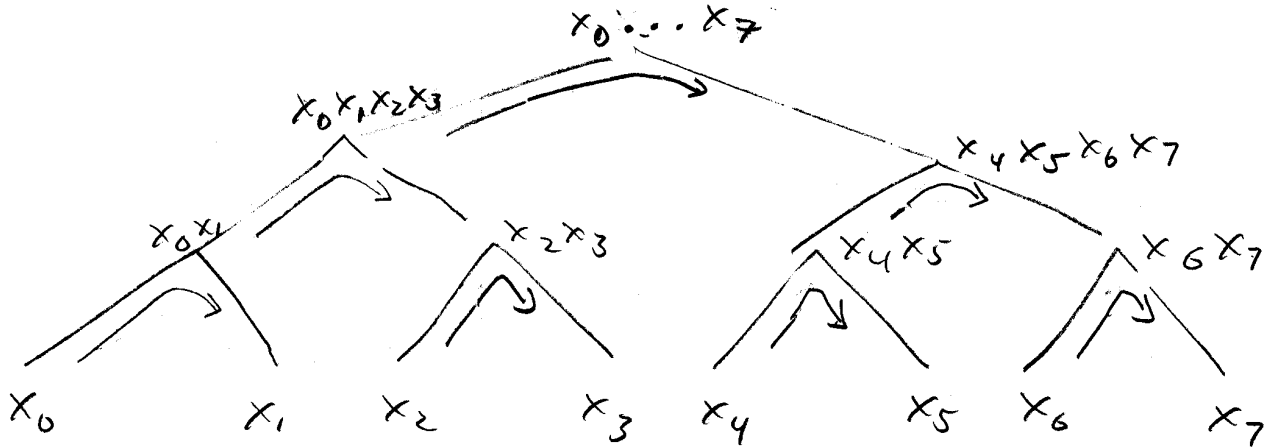

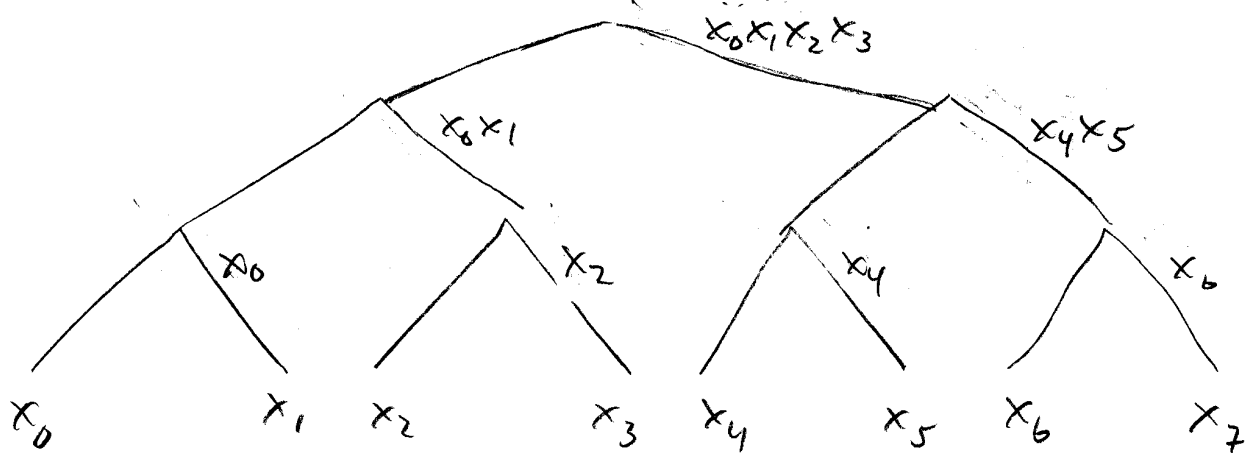Left child values are passed up and right



Postscript Kill, propagate, generate first used in Harvard relay calculator circa mid-1940's.

$O(1)$ -time addition (in their model).